

Code No: 20CS3301/20IT3301

PVP SIDDHARTHA INSTITUTE OF TECHNOLOGY
(Autonomous)

20CS3301/20IT3301-Fundamentals of Digital Logic Design
(Common to CSE, IT)

Duration: 3 Hours**Max. Marks: 70****Note:**

1. This question paper contains 5 essay questions with an internal choice.
2. Each question carries 14 Marks.
3. All parts of Question paper must be answered in one place

5 x 14 = 70 Marks

			Blooms Level	CO	Max. Marks
UNIT-I					
1	(a)	Convert the following base conversions using Number System i. $(53.625)_{10}$ to $(?)_2$ ii. $(3FD)_{16}$ to $(?)_2$ iii. $(A69.8)_{16}$ to $(?)_{10}$	L2	CO1	7M
	(b)	Perform the decimal subtraction in 8-4-2-1 BCD using 9's complement. i) Subtract 79 from 26 ii) Subtract 748 from 983.	L2	CO1	7M
OR					
2	(a)	Show the Gray code for the following decimal numbers. i) 37_{10} ii) 97_{10} .	L2	CO1	7M
	(b)	Explain the various logic gates and give the representation along with the truth tables.	L2	CO1	7M
UNIT-II					
3	(a)	Obtain the simplified expression in SOP form of $F(a, b, c, d, e) = \sum(1,2,4,7,12,14,15,24,27,29,30,31)$ using K-maps.	L3	CO2	7M
	(b)	Simplify the following Boolean functions, using a four variable Karnaugh map method and implement the simplified function using NAND gates $F(A,B,C,D) = \sum(0,2,4,5,6,7,8,10,13,15)$	L3	CO2	7M
OR					
4	(a)	Obtain the simplified expression in product of sums) using K-maps i) $F(A,B,C,D) = \pi(0,1,2,3,4,10,11)$ ii) $F(A,B,C,D) = \pi(1,3,5,7,13,15)$	L3	CO2	7M
	(b)	With the use of K-Map method to simplify the following Boolean expression. $F(w, x, y, z) = \sum(2, 3, 5, 6, 11, 14, 15)$	L3	CO2	7M

UNIT-III					
5	(a)	Construct the truth table of 3 bit gray to binary code conversion. Show the realization using 4X1 MUX?	L3	CO3	7M
	(b)	Design a full binary adder with the use of two half adders and a OR gate.	L3	CO3	7M
OR					
6	(a)	Design an 8-bit BCD adder using 4-bit binary adder.	L3	CO3	7M
	(b)	Implement the full adder using two 4:1 multiplexers.	L3	CO3	7M
UNIT-IV					
7	(a)	Design the conversion logic to convert SR Flip-Flop into JK Flip-Flop.	L3	CO3	7M
	(b)	Compare combinational and sequential circuits.	L4	CO4	7M
OR					
8	(a)	Construct the D and T flip flop with logic diagrams and function table.	L3	CO3	7M
	(b)	Distinguish between the SR Flip Flop and JK Flip Flop.	L4	CO4	7M
UNIT-V					
9	(a)	Design a BCD ripple counter using JK flip-flop.	L3	CO3	7M
	(b)	Design a three bit counter that counts up when a control variable E = 0 and counts down when E = 1.	L3	CO3	7M
OR					
10	(a)	Design a 4-bit ripple counter and draw the timing diagram of that counter.	L3	CO3	7M
	(b)	Design a four-bit binary synchronous counter with D flip-flops	L3	CO3	7M

Course Coordinators

1. Dr G Lalitha Kumari
2. Dr B Lakshmi Ramani
3. Mr P Anil Kumar

Course Coordinators

1. Dr. K. Pavan Kumar

Prof. & Head, Dept. of CSE

(Dr. A. Jaya Lakshmi)

Prof. & Head, Dept. of IT

(Dr B.V. Subba Rao)